

MAVEN SILICON HACKATHON LEVEL 2


Submitted by

P.NIRANJAN – 2022105040

Mail:niranjuviky@gmail.com

Phone:6381654696

 ELECTRONICS AND COMMUNICATION ENGINEERING



**COLLEGE OF ENGINEERING, GUINDY
CHENNAI -600025**


AIM

To design a sequence detector that detects the overlapping sequence “10101” from the input datastream with MSB detected first using Moore State Machine.


SOFTWARE REQUIRED

Xilinx Vivado

STATE DIAGRAM:

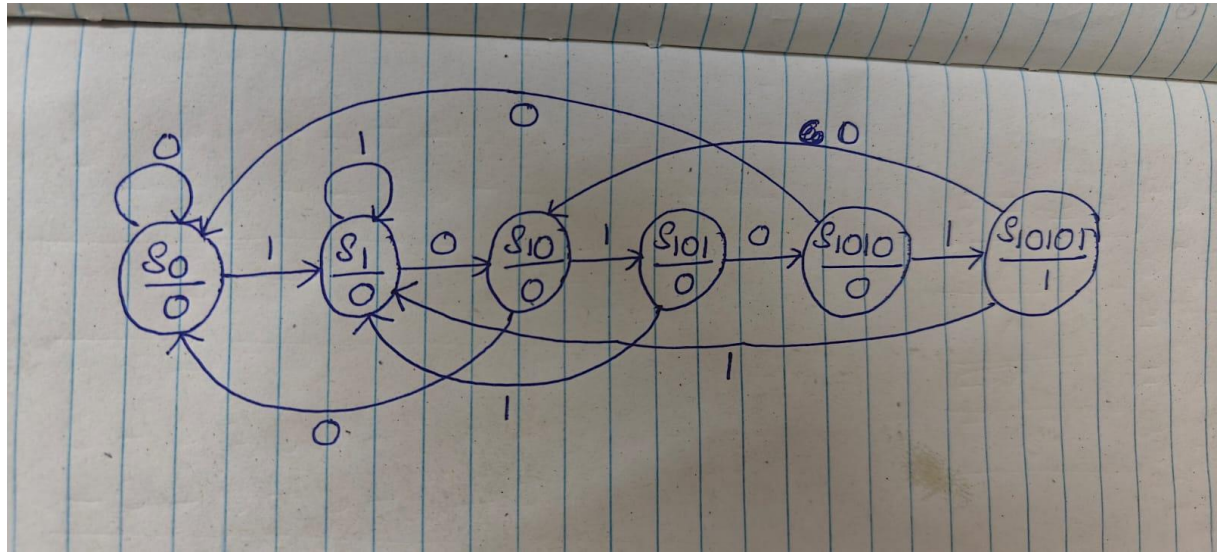

EXPECTED WAVEFORM:

 

VERILOG CODE:

```
`timescale 1ns / 1ps
```

```
module Sequence_10101_detector(  
    input clk,  
    input reset,  
    input input_data,  
    output reg sequence_detected  
);  
    parameter S0    = 3'b000,  
              S1    = 3'b001,  
              S10   = 3'b010,  
              S101  = 3'b011,  
              S1010 = 3'b100,  
              S10101 = 3'b101;  
  
    reg [2:0] state, next_state;  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            state <= S0;  
        else  
            state <= next_state;  
    end  
  
    always @(*) begin  
        case (state)  
            S0:    next_state = input_data ? S1 : S0;  
            S1:    next_state = input_data ? S1 : S10;  
            S10:   next_state = input_data ? S101 : S0;  
            S101:  next_state = input_data ? S1 : S1010;  
            S1010: next_state = input_data ? S10101 : S0;  
            S10101: next_state = input_data ? S1 : S10;  
            default: next_state = S0;  
        endcase  
    end  
  
    always @(*) begin  
        sequence_detected = (state == S10101);  
    end  
  
endmodule
```

TEST BENCH:

```
`timescale 1ns / 1ps

module Sequence_10101_detector_tb;


    reg clk;
    reg reset;
    reg input_data;
    wire sequence_detected;

    // Instantiation
    Sequence_10101_detector uut (
        .clk(clk),
        .reset(reset),
        .input_data(input_data),
        .sequence_detected(sequence_detected)
    );


    always #5 clk = ~clk;

    initial begin
        clk = 0;
        reset = 1;
        input_data = 0;
        #10;
        reset = 0;
        #10 input_data = 1;
        #10 input_data = 0;
        #10 input_data = 1;
        #10 input_data = 0;
        #10 input_data = 1; // (sequence_detected = 1)
        #10 input_data = 0;
        #10 input_data = 1;
        #10 input_data = 0;
```

RTL SCHEMATIC:

 

SYNTHESIS:

 

RESULT:

The sequence detector has been implemented using a Moore state machine logic. The corresponding Verilog code and testbench were developed, simulated, and successfully verified.